

Digital Design with VHDL

CSE 560M

Lecture 5


Shakir James

Plan for Today

- Announcement
 - Commentary due Wednesday
 - HW1 assigned today. **Begin immediately!**
- Questions
- VHDL help session
- Assignment

Design Entity

 - Hardware abstraction
- Entity definition
 - entity declaration
 - architecture body



Entity and Architecture

```
entity and2 is  
  port (x , y: in std_logic;  
        f: out std_logic);
```


```
end and2;
```

```
architecture a1 of and2 is  
begin
```

```
  process (x, y)  
  begin  
    f <= x and y;  
  end process;
```

```
end a2;
```
 
```
architecture a2 of and2 is  
begin  
  f <= '1' when a='1' and b='1' else  
    '0';  
end a1;
```



- Entity declaration
 - inputs and outputs
- Architecture body
 - Process description
 - Structural description

} Concurrent assignment
(“same” as process)

Multiple Assignments

- Concurrent region
 - a “wire”

```
architecture a1 of e is
begin
  x <= '0';
  y <= x;
  x <= '1';
end a1;
```



```
x = 'X';
y = 'X';
```

- Within a process
 - “pseudo-sequential”



```
architecture a2 of e is
begin
  p: process (x, y)
  begin
    x <= '0';
    y <= x;
    x <= '1';
  end process;
end a2;
```



```
x = '1';
y = '1';
```

Structural Description
  
```
entity and4 is
  port (i0,i1,i2,i3: in std_logic;
        f: out std_logic);
end and4;
```



```
architecture circuit of and4 is
```



```
  component and2
    port (x,y : in std_logic;
          f   : out std_logic);
  end component;
```

```
  signal n1, n2: std_logic;
```

```
begin
  a2_1: and2 port map (i0,i1,n1);
  a2_2: and2 port map (i2,i3,n2);
  a2_3: and2 port map (n1,n2,f)
end circuit;
```

Process Description
  
```
entity and4 is  
  port (i0,i1,i2,i3: in std_logic;  
         f: out std_logic);  
end and4;
```



```
architecture a2 of and4 is  
  signal n1,n2: std_logic;  
begin
```

```
  p: process (i0,i1,i2,i3,n1,n2)  
  begin  
    n1 <= a and b;  
    n2 <= c and d;  
    f <= n1 and n2;  
  end process;
```

```
end a2;
```

Combinatorial and Sequential

	Combinatorial Logic	Sequential Logic
State	No	Yes
Examples	<ul style="list-style-type: none">•Logic functions•Arithmetic functions•Multiplexers•Decoders	<ul style="list-style-type: none">•Latches•Flip-flops•Registers•Counters
Architecture	<ul style="list-style-type: none">•Processes•Concurrent statements	<ul style="list-style-type: none">•Processes

Concurrent statements are simpler!

Combinatorial Logic as Process

- Common error #1

```
entity and3 is
  port (a, b, c: in std_logic;
        f: out std_logic);
end and3;
```

```
architecture a of and3 is
begin
  p: process(a, b)
  begin
    o <= a and b and c;
  end process;
end a;
```


c missing in sensitivity list

- Common error #2

```
architecture a of e is
begin
  p: process(a, b)
  begin
    if a = '0' then
      x <= a; y <= b;
    elsif a = b then
      x <= '0'; y <= '1';
    else
      x <= not a;
    fi
  end process;
end a;
```

y not defined in else

Clocked Sequential Circuit

 

```
entity fsm is
  port (x, rst_l, clk: in std_logic;
        z : out std_logic);
end fsm;

architecture mealy of fsm is
  type states is (s0, s1);
  signal state: states := s0;
begin
```

```
state_trans: process (clk)
begin
  if (rising_edge(clk)) then
    if (rst_l= '0') then
      state <= s0;
    else
      case state is
        when s0 => if (x = '1') then
                    state <= s1;
                  end if;
        when s1 => if (x = '1') then
                    state <= s0;
                  end if;
      end case;
    end if;
  end process state_trans;

  -- code that defines outputs
  z <= '1' when (state = s0 and x = '1')
        or (state = s1 and x = '0')
        else '0';

end mealy;
```

Assignment

- HW1 assigned, due 9/23
- Readings
 - For Wednesday
 - H&P: Appendix A, sections A3- A.5
 - **Commentary:** *Retrospective on HLL Computers*
 - submit commentary to newsgroup before class
 - For Monday
 - H&P: Appendix A, sections A6- A.9
 - V&L: Ch. 4

Exercise 1

- Write a VHDL module implementing a 4 input multiplexer. Each input should be a 32 bit wide `std_logic_vector`.
- Hint
 - Entity:
 - inputs:
 - outputs:
 - Architecture:
 - combinatorial or sequential logic?

Exercise 1 - Solution

```
library ieee;
use ieee.std_logic_1164.all;

entity mux is
    port (p0,p1,p2,p3: in  std_logic_vector(31 downto 0);
          sel          : in  std_logic_vector(1 downto 0);
          output       : out std_logic_vector(31 downto 0));
end mux;

architecture beh of mux is
begin
    output <= p0 when sel="00" else
              p1 when sel="01" else
              p2 when sel="10" else
              p3 when sel="11";
end beh;
```

Exercise 2

- Write a VHDL module implementing a **synchronous** 32 bit counter. A “**reset**” signal resets the counter to 0. An “**en**” signal enables the counter modification. An “**up**” signal indicates whether the counter must be incremented (1)/decremented(0).
- The output of the module is the value of the signal, represented as 32 bit wide `std_logic_vector`.

Exercise 2 - Solution

```
library ieee;
use ieee.std_logic_1164.all;

entity mux is
    port (p0,p1,p2,p3: in  std_logic_vector(31 downto 0);
          sel      : in  std_logic_vector(1 downto 0);
          output   : out std_logic_vector(31 downto 0));
end mux;

architecture beh of mux is
begin
    output <= p0 when sel="00" else
              p1 when sel="01" else
              p2 when sel="10" else
              p3 when sel="11";
end beh;
```

Exercise 2 - Solution (cont'd)

```
architecture beh of counter is
    signal count : integer;
begin
    counter_p: process(clk)
    begin
        if (rising_edge(clk)) then
            if (reset = '1') then
                count <= 0;
            else
                if en = '1' then
                    if up = '1' then
                        count <= count + 1;
                    else
                        count <= count - 1;
                    end if;
                end if;
            end if;
        end if;
    end process;

    output <= conv_std_logic_vector(count,32);
end beh;
```

Exercise 3

- Use the modules written for exercises 1 and 2 in order to implement a **synchronous** register file containing 4 counters. The multiplexer will allow to determine which counter will be seen on the **single output**.
- The module should present a global **reset** signal, a **write enable** signal, a **read and a write selector**, and an **up** signal.

Exercise 3 - Solution

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity counter_reg is
  port (clk      : in std_logic;
        write_en : in std_logic;
        up       : in std_logic;
        reset    : in std_logic;
        read_sel : in std_logic_vector(1 downto 0);
        write_sel: in std_logic_vector(1 downto 0);
        output   : out std_logic_vector(31 downto 0));
end counter_reg;

architecture struct of counter_reg is

  component mux
    port (p0,p1,p2,p3: in  std_logic_vector(31 downto 0);
          sel       : in  std_logic_vector(1 downto 0);
          output    : out std_logic_vector(31 downto 0));
  end component;

  component counter
    port (clk      : in std_logic;
          en       : in std_logic;
          up       : in std_logic;
          reset    : in std_logic;
          output   : out std_logic_vector(31 downto 0));
  end component;
```

Exercise 3 - Solution (cont'd)

```
begin
```

```
    wr_en    <= "0000" when write_en = '0' else  
              "0001" when write_sel="00" else  
              "0010" when write_sel="01" else  
              "0100" when write_sel="10" else  
              "1000";
```

```
    cloop: for i in 3 downto 0 generate  
        cnt: counter port map (clk, wr_en(i), up, reset, outputs(i));  
    end generate;
```

```
    m: mux port map (outputs(0), outputs(1), outputs(2), outputs(3),  
                    read_sel, output);
```

```
end struct;
```